





Tanta University

Faculty of Engineering

Electrical Power and Machines Engineering Department



First Year – Second Term

(Electrical Power and Machines Engineering Department)

Course Title

Electrical Circuits (2)

EPM1203

(3+2)

Dr. Said M. Allam



Part 2

Balanced Three-Phase Circuits





Lecture Outlines

- ☐ Generating Single-Phase Voltage
- ☐ Generating Three-Phase Voltages
- ☐ Importance of Three-Phase System
- ☐ Three-Phase Generator
- ☐ Basic Three-Phase Circuit
- ☐ Y-Y Three-Phase System
- ☐ Solved Example on Y-Y System



Generating Single-Phase Voltage

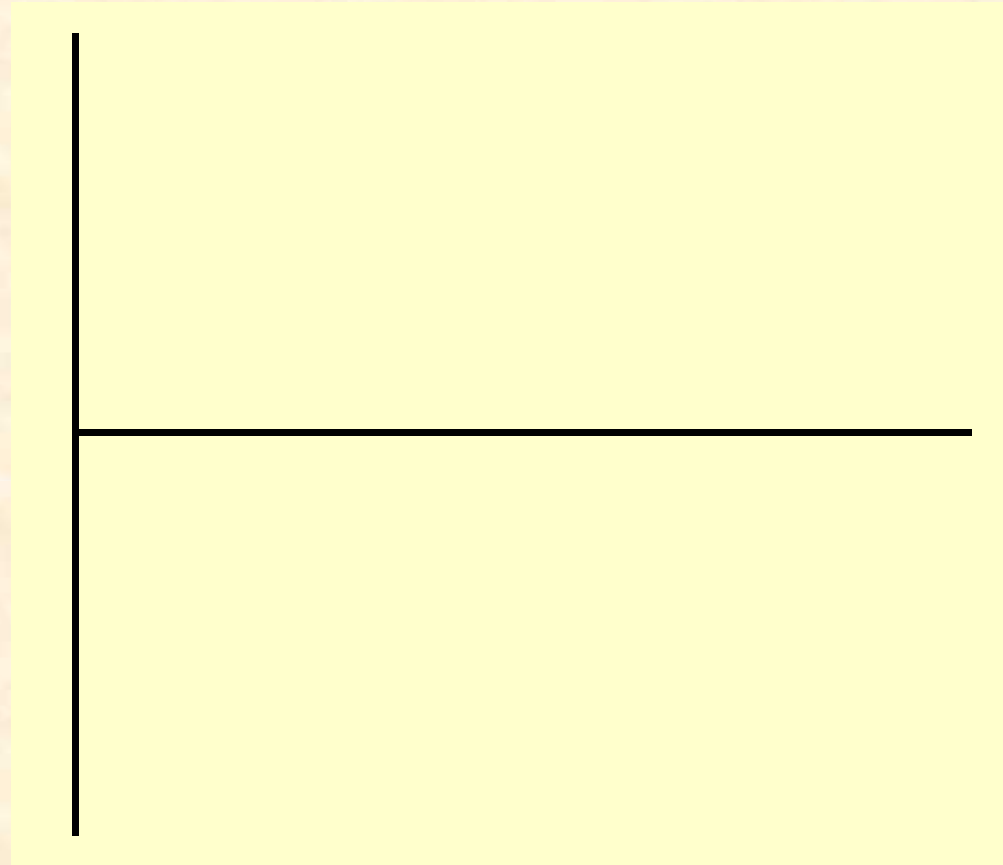
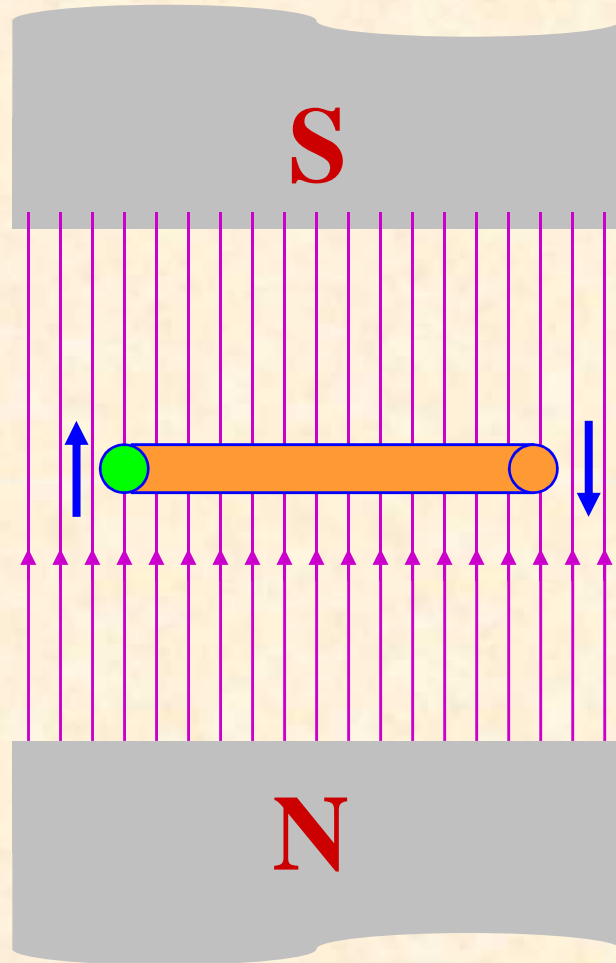


Motion is parallel to the flux

No voltage is induced



Generating Single-Phase Voltage

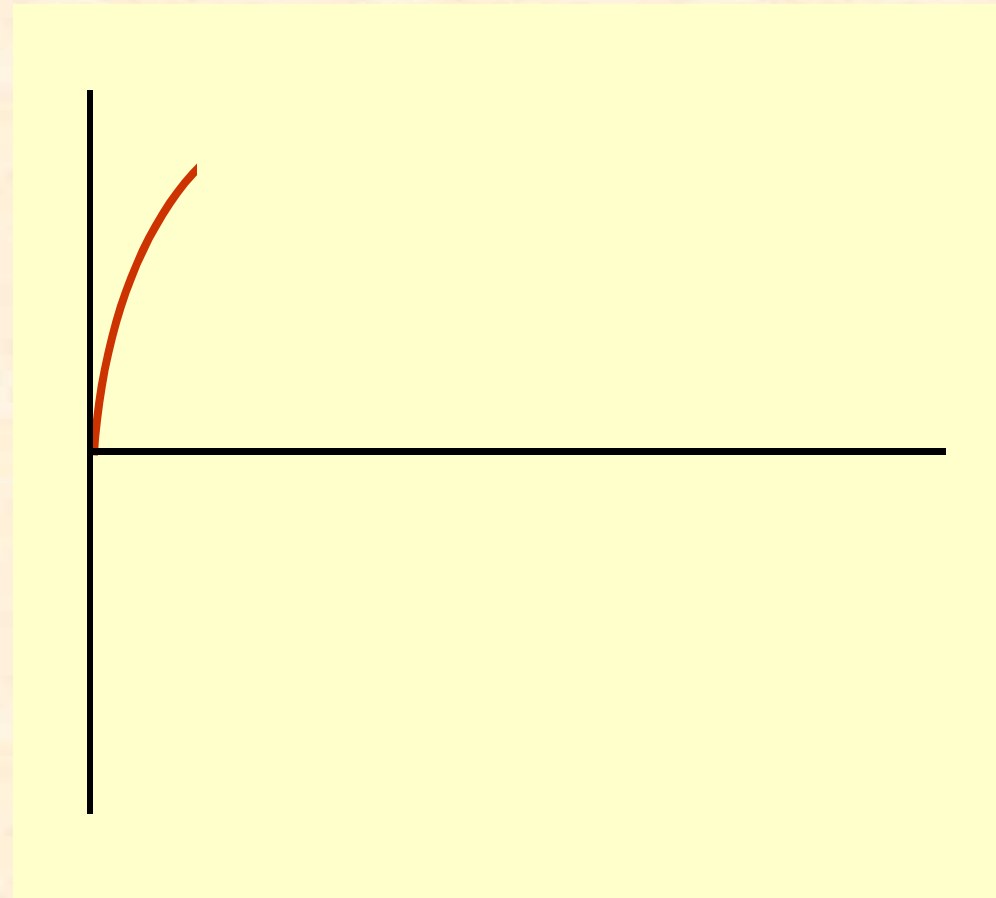
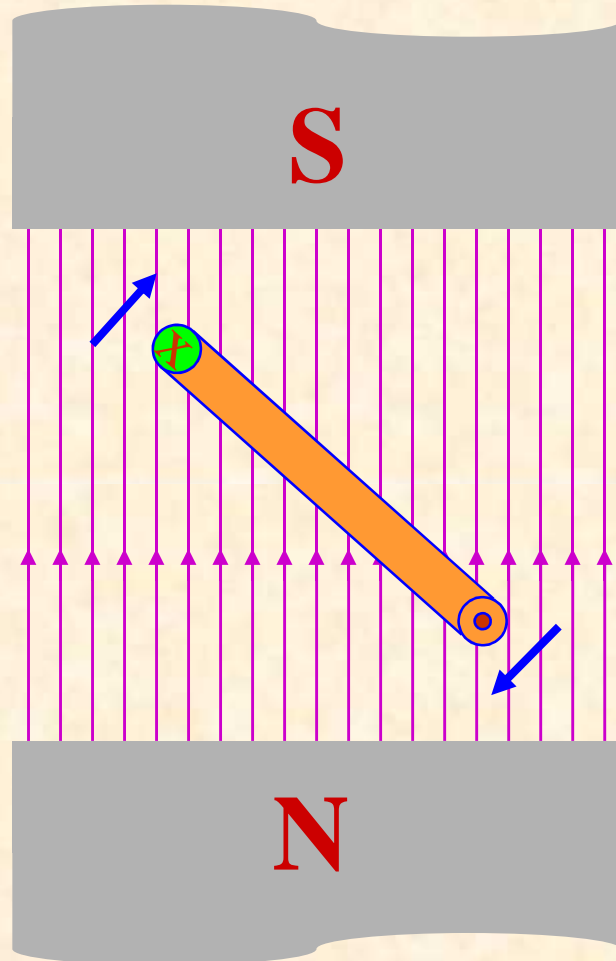


Motion is 45° to flux

Induced voltage is 0.707 of maximum





Generating Single-Phase Voltage

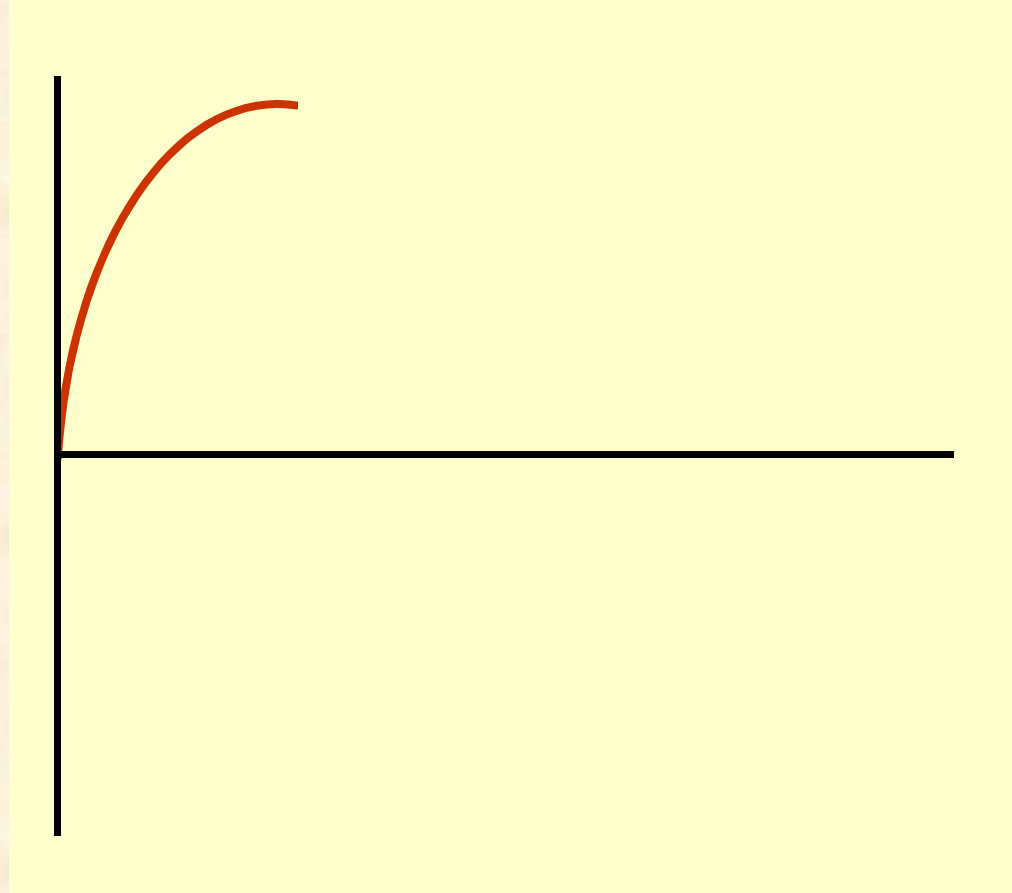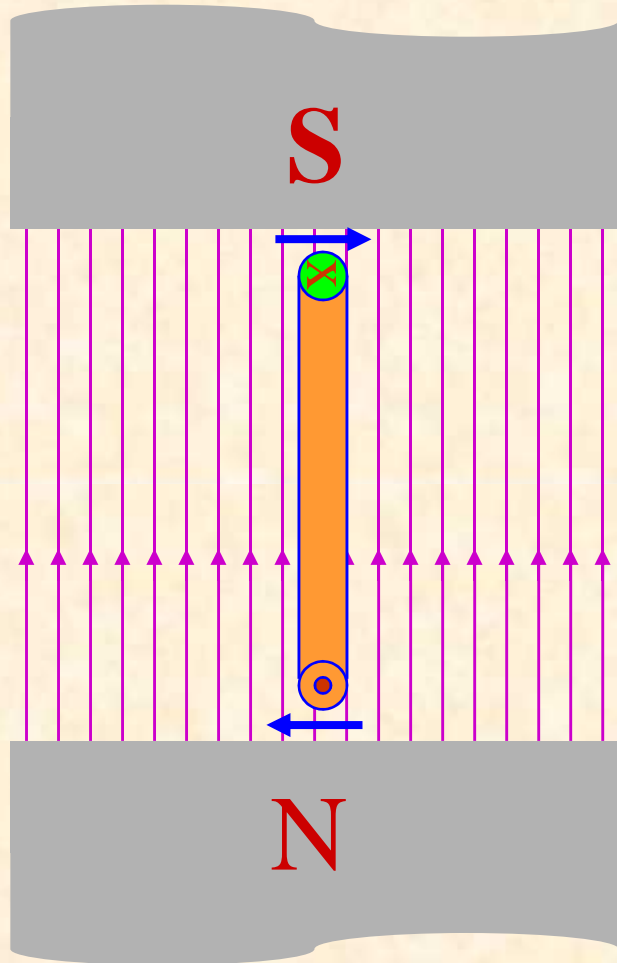

Motion is perpendicular to flux
Induced voltage is maximum





Generating Single-Phase Voltage

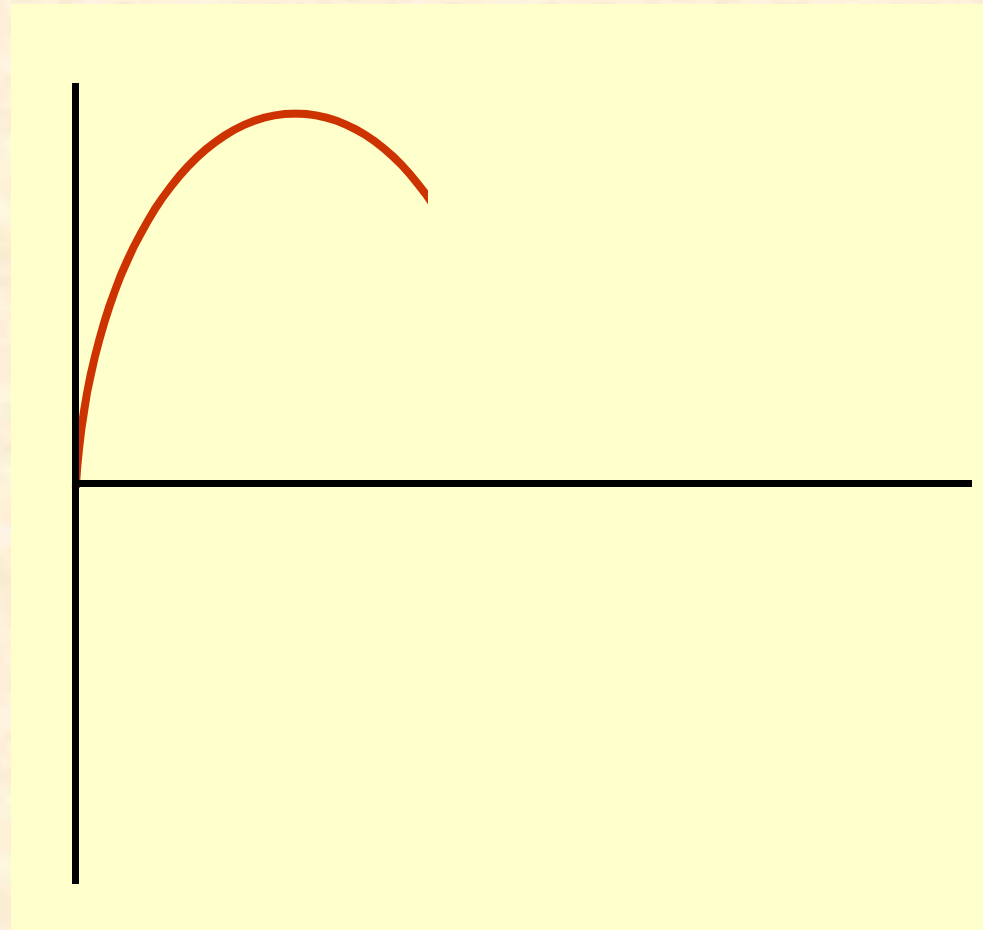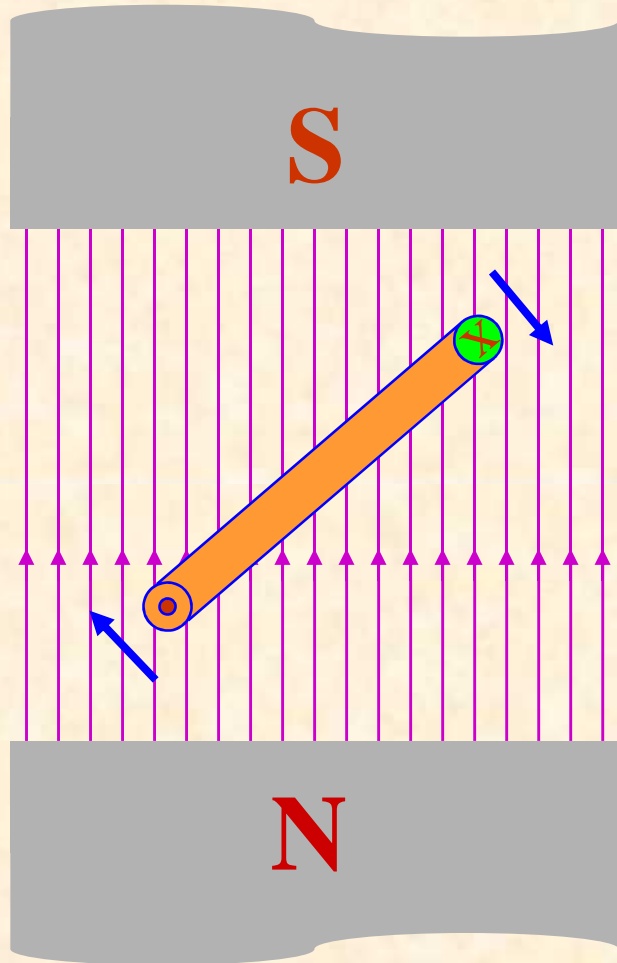

Motion is 45° to flux
Induced voltage is 0.707 of maximum




Generating Single-Phase Voltage

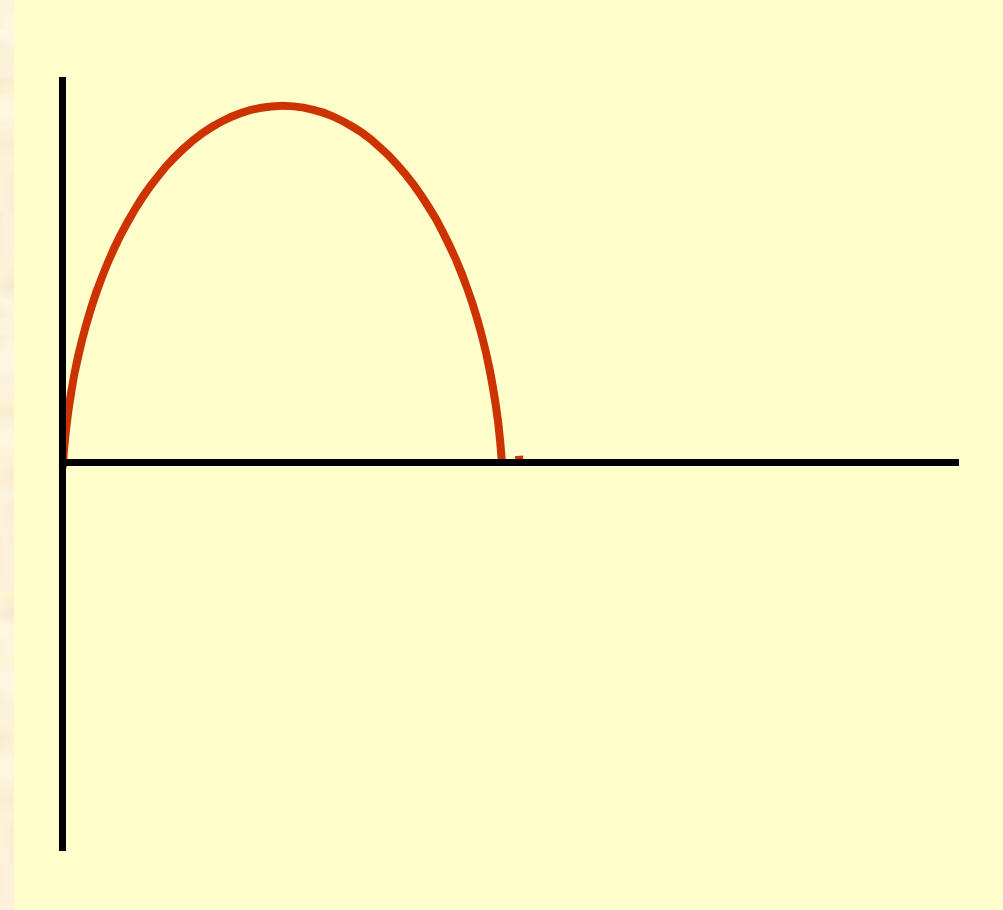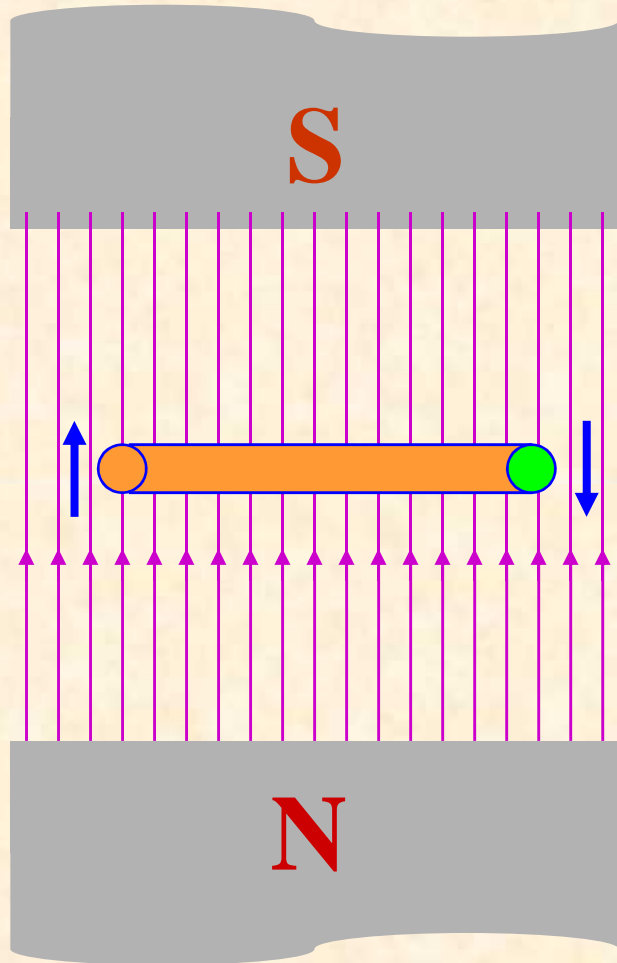


Motion is parallel to flux
No voltage is induced



Generating Single-Phase Voltage

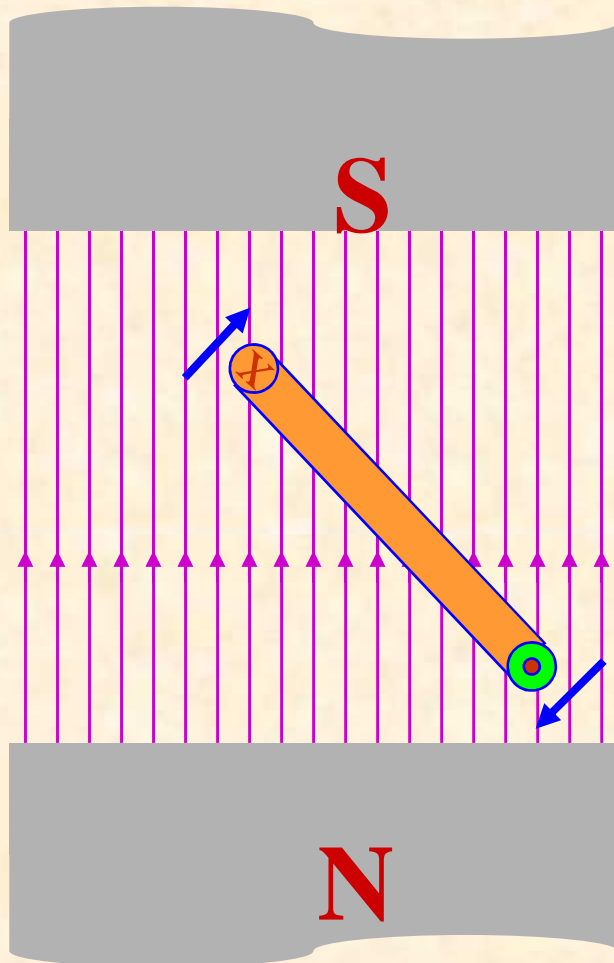


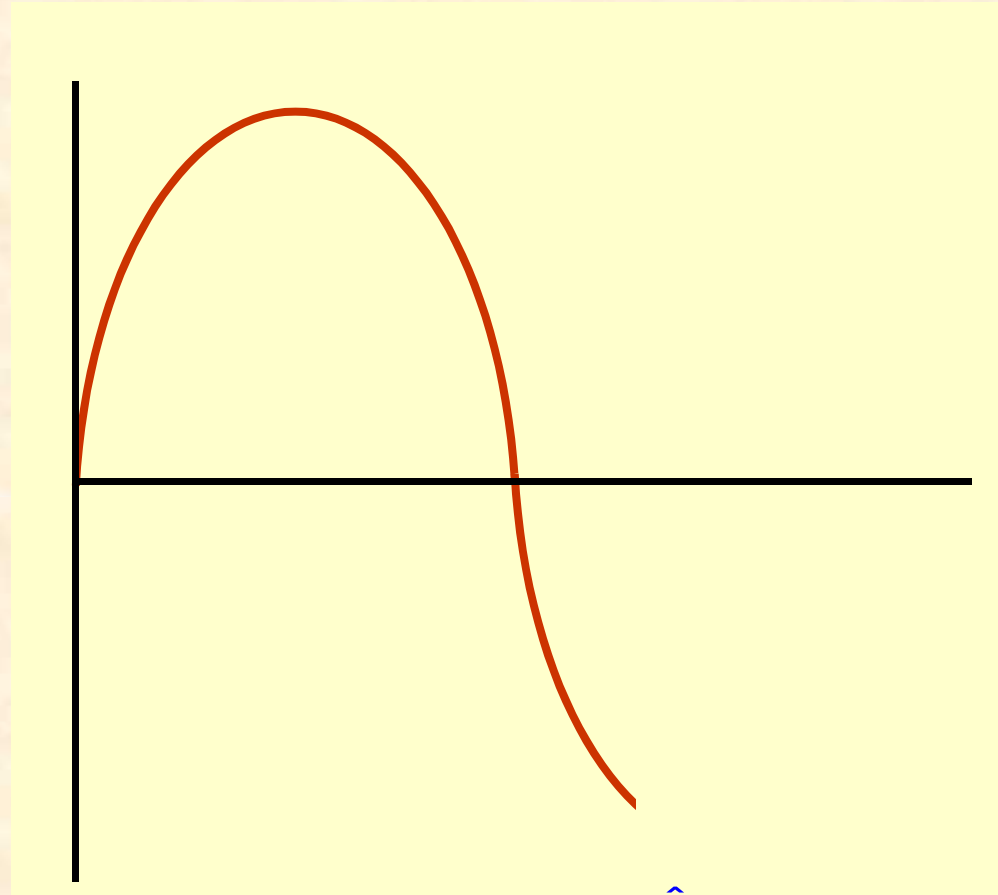
**Notice current in the
conductor has reversed**



**Motion is 45° to flux
Induced voltage is
0.707 of maximum**





Generating Single-Phase Voltage

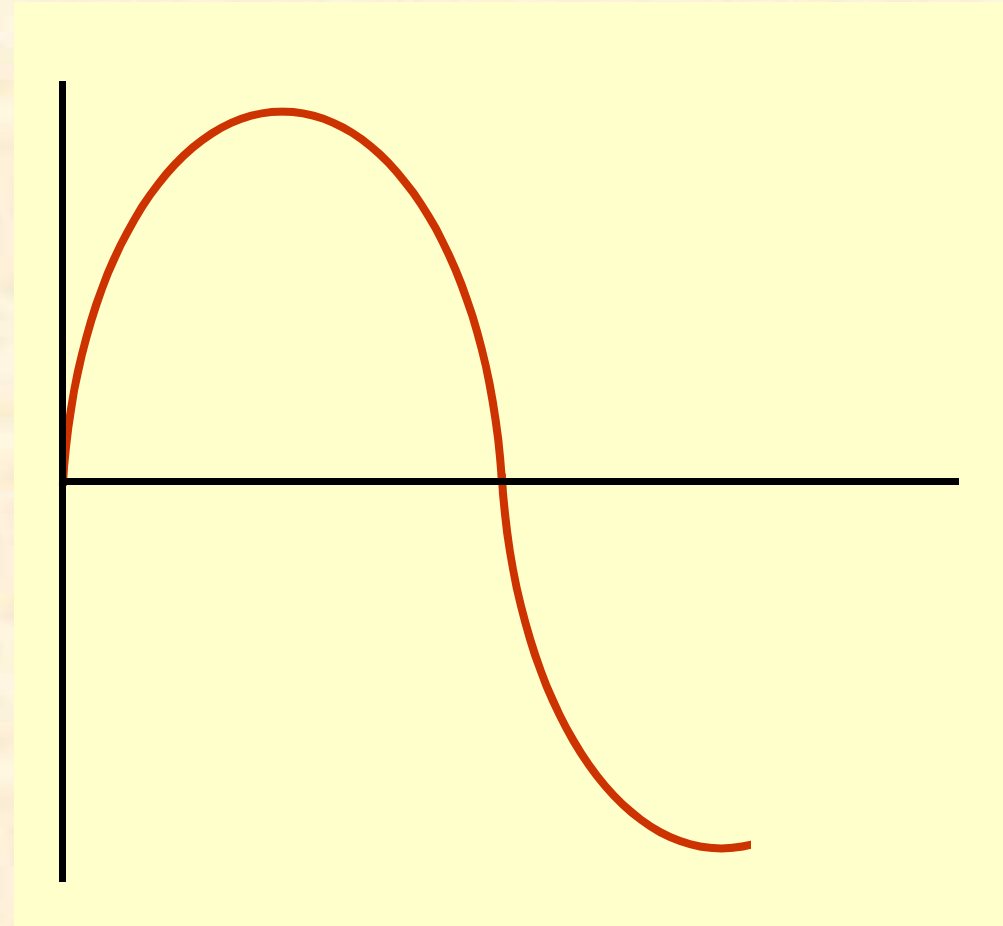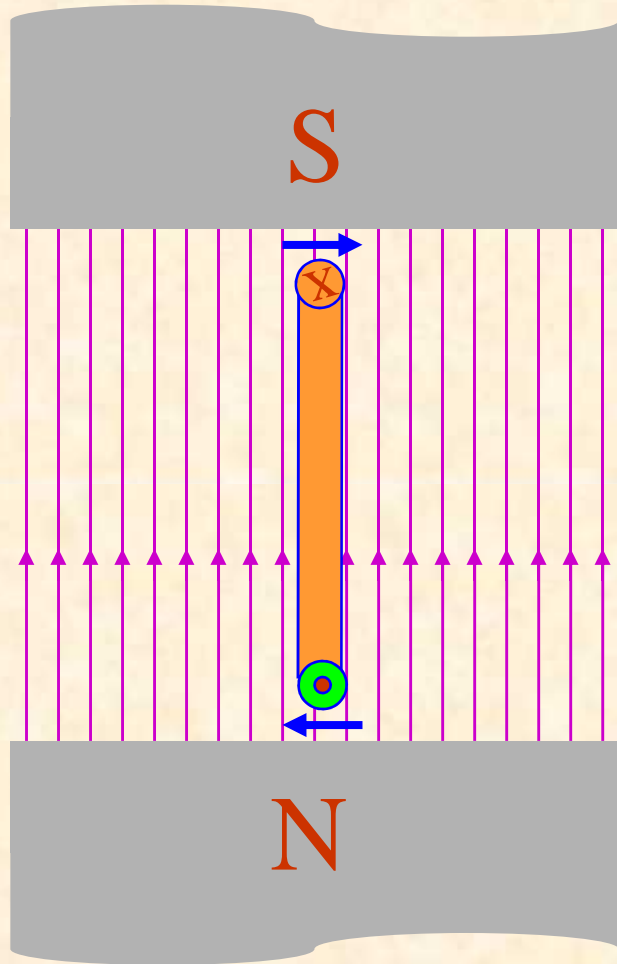

Motion is perpendicular to flux
Induced voltage is maximum



Generating Single-Phase Voltage

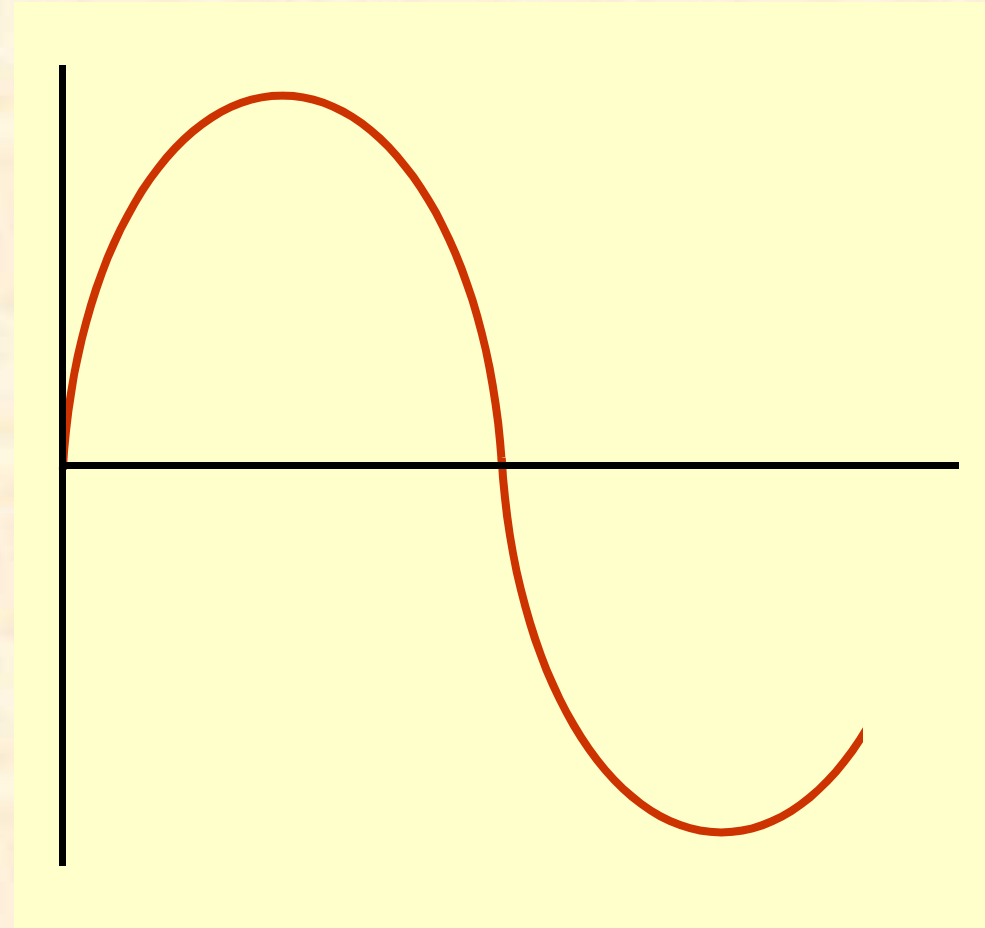
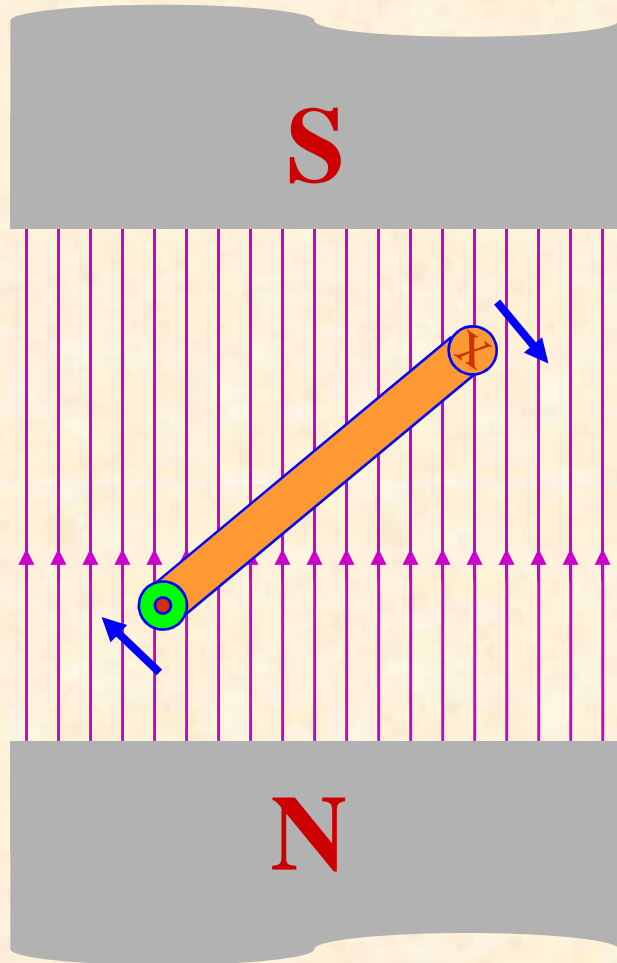


Motion is 45° to flux

Induced voltage is 0.707 of maximum



Generating Single-Phase Voltage

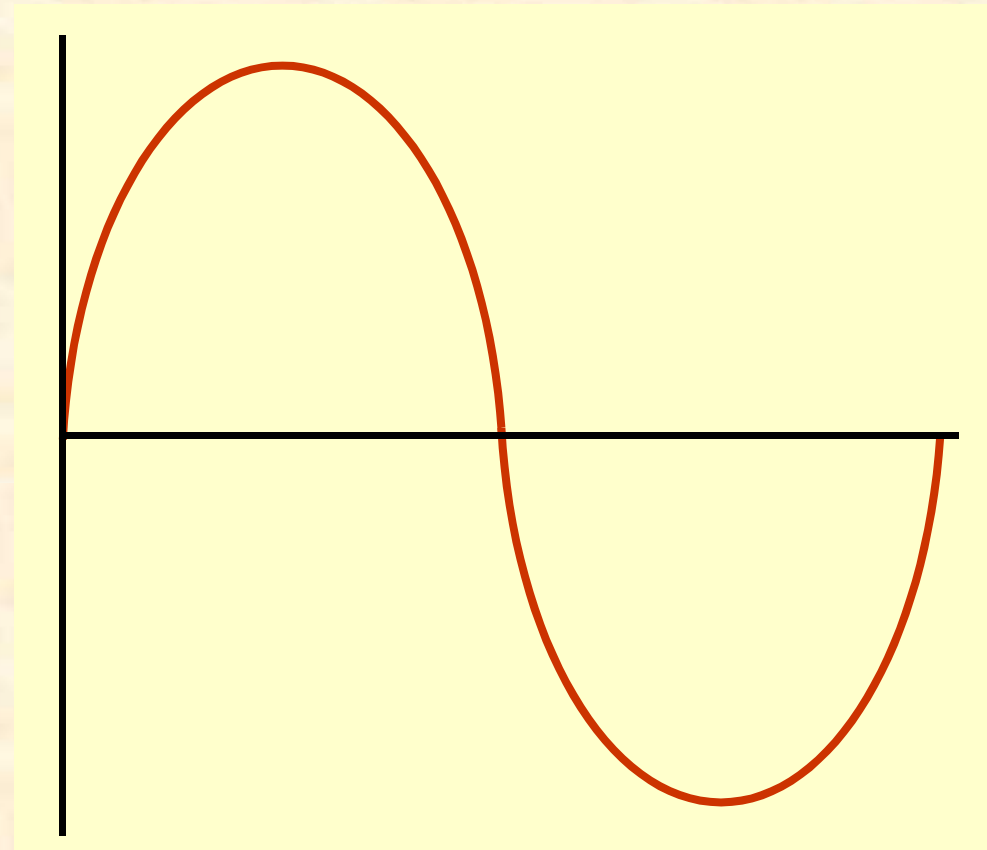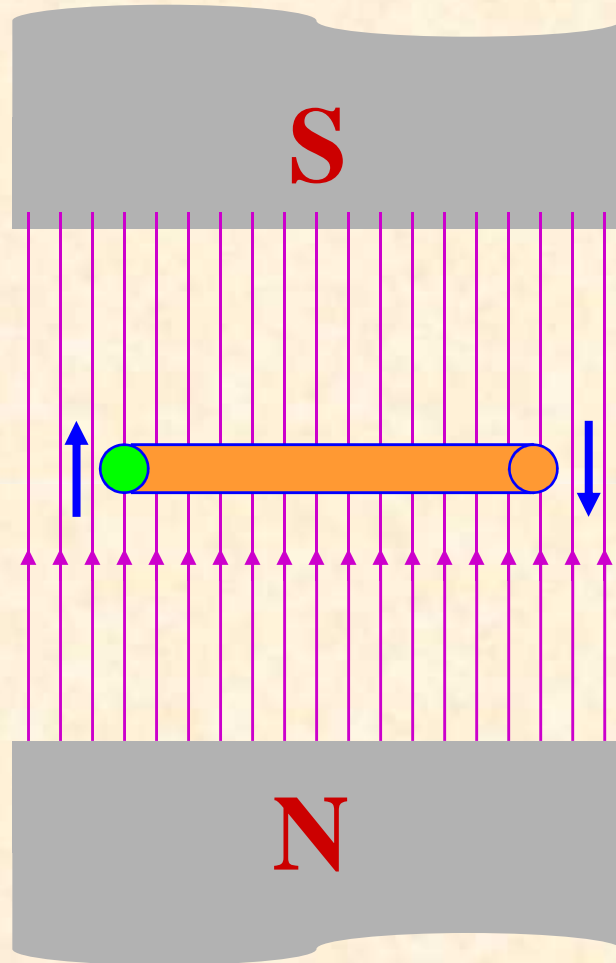


Motion is parallel to flux
No voltage is induced

Ready to produce another cycle




Generating Three-Phase Voltage


Phase-a Phase-b Phase-c

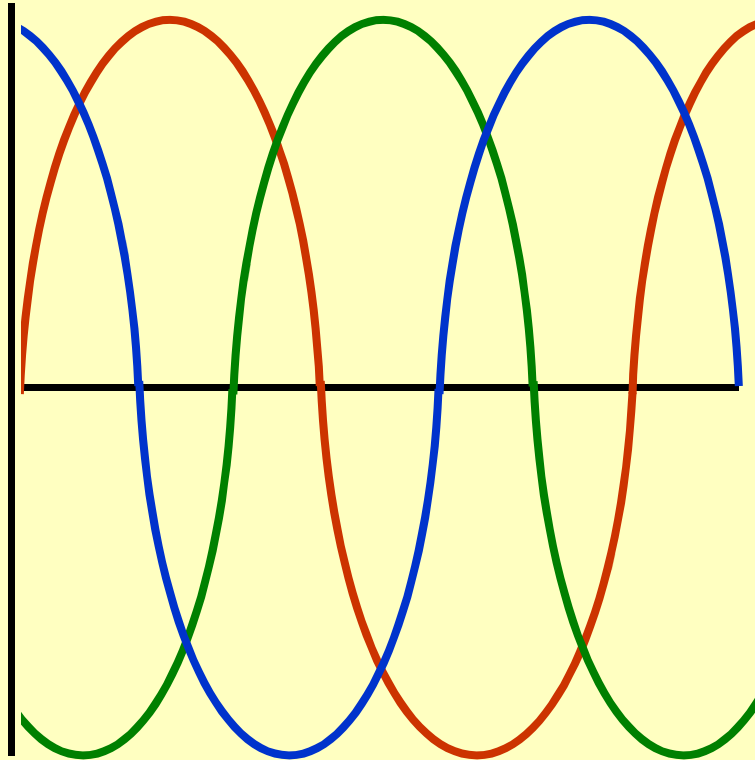

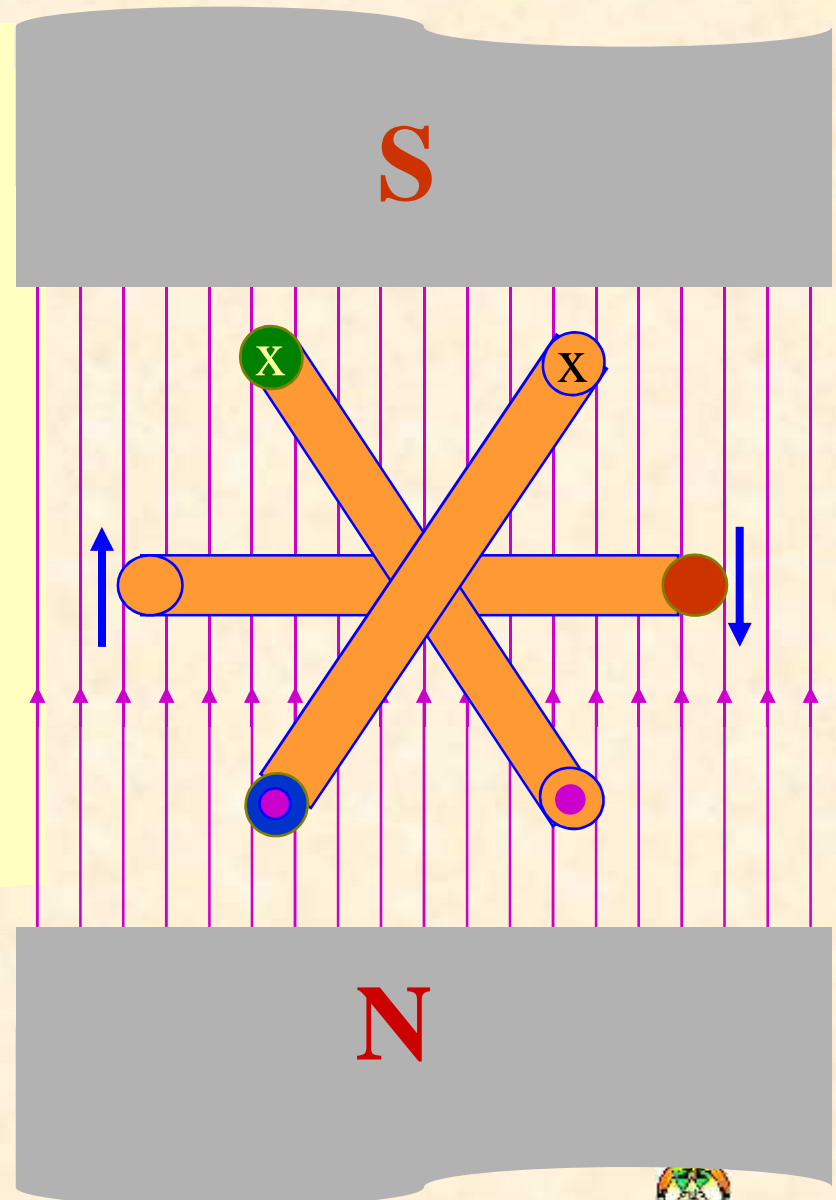Phase-a is ready to go positive
Phase-b is going more negative
Phase-c is going less positive



Generating Three-Phase Voltage

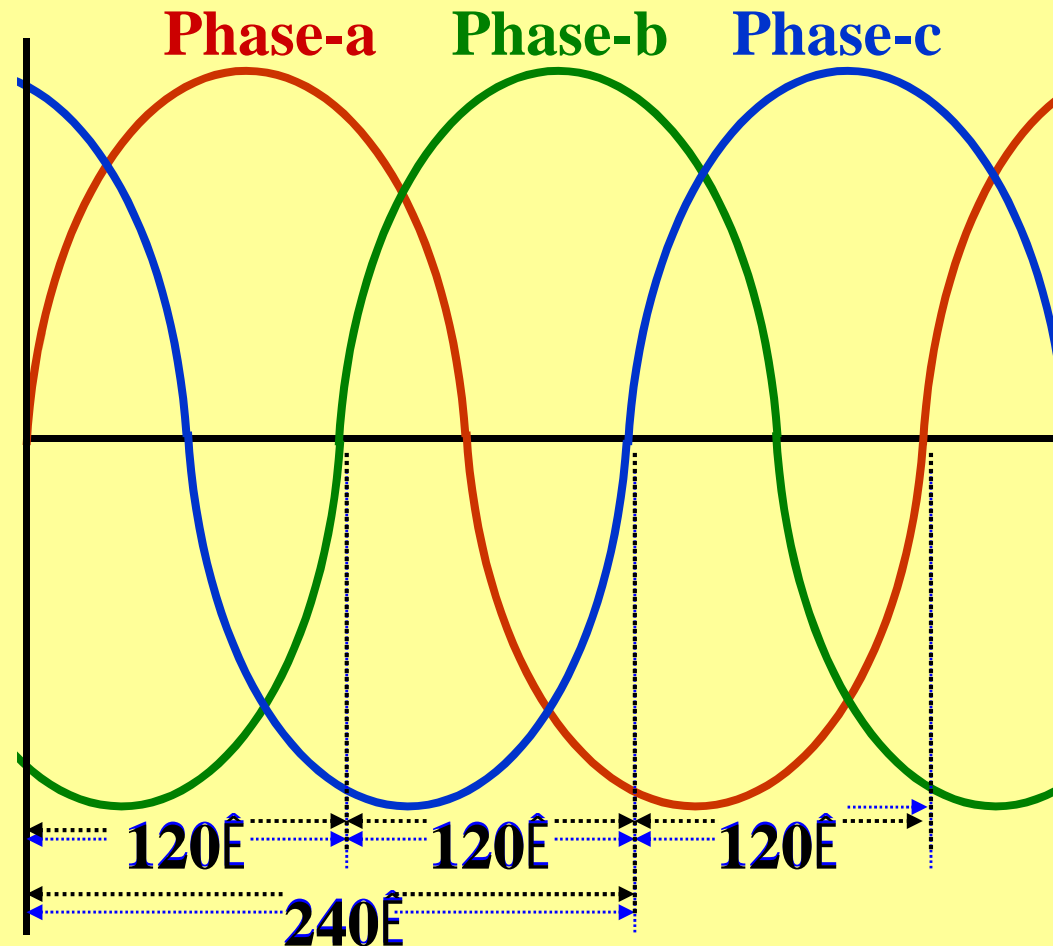

Phase-b lags phase a by 120°
Phase-c lags phase a by 240°

Phase-b leads phase c by 120°
Phase-a leads phase c by 240°



Importance of Three-Phase System

- ❑ All electric power is generated and distributed in three phase
- ✓ One phase and two phase, can be taken from three-phase system rather than generated independently
- ✓ The **instantaneous power** in a 3ϕ system can be **constant** (not pulsating)
- ✓ High power motors prefer a **steady torque** especially one created by a rotating magnetic field
- ✓ Three-phase system is **more economical** than the single phase
- ✓ The **amount of wire** required for a three phase system is **less than** required for an equivalent single-phase system




Three-Phase Generator

- The **generator** consists of a rotating magnet (**rotor**) surrounded by a stationary winding (**stator**)
- Three separate windings or coils with terminals a-a', b-b', and c-c' are physically placed 120° apart around the stator
- **As the rotor rotates**, its magnetic field cuts the three coils and induces voltages in the coils
- The **induced voltage** have equal magnitude but out of phase by 120°




Three-Phase Generator

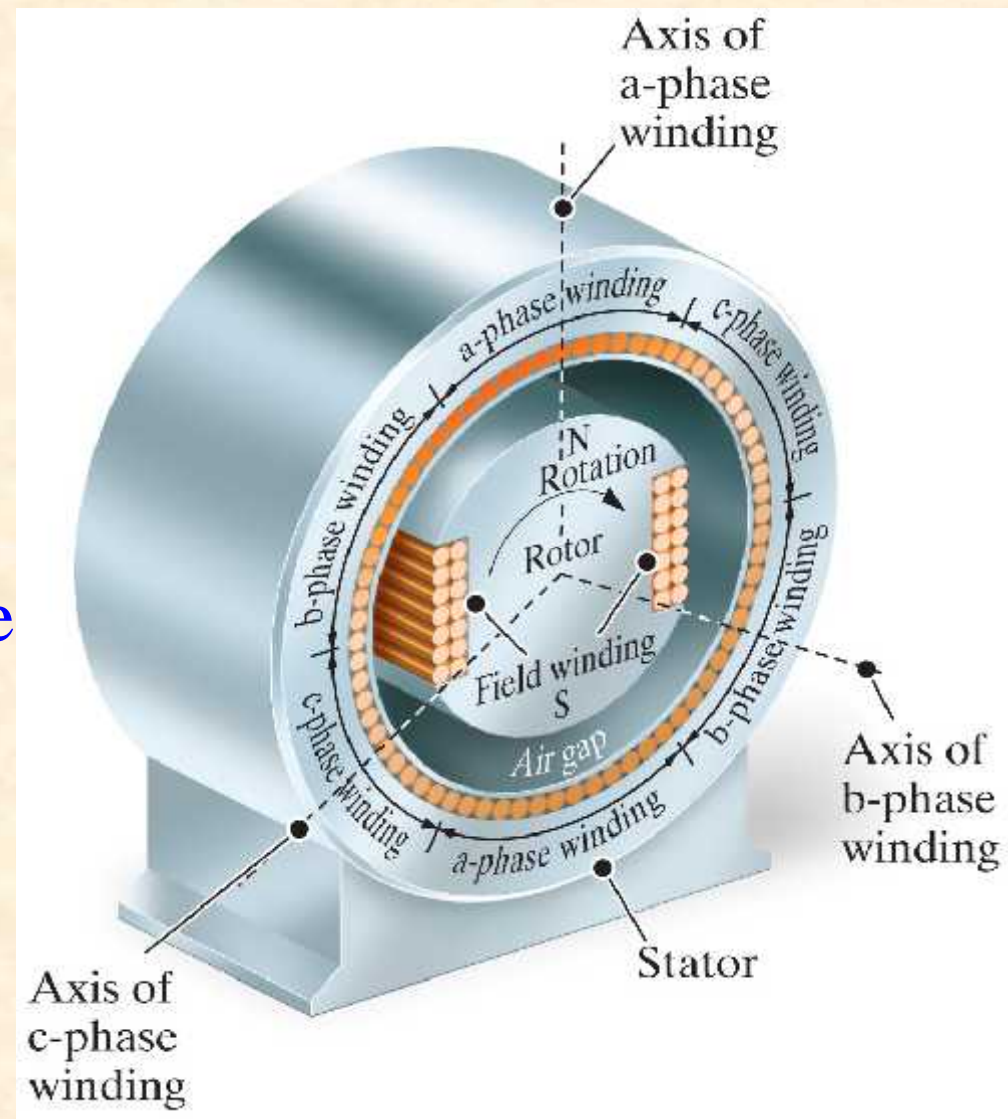
- ✓ 2-pole (North-South) rotor turned by a “prime mover”
- ✓ Sinusoidal voltages are induced in each stator winding




Three-Phase Generator

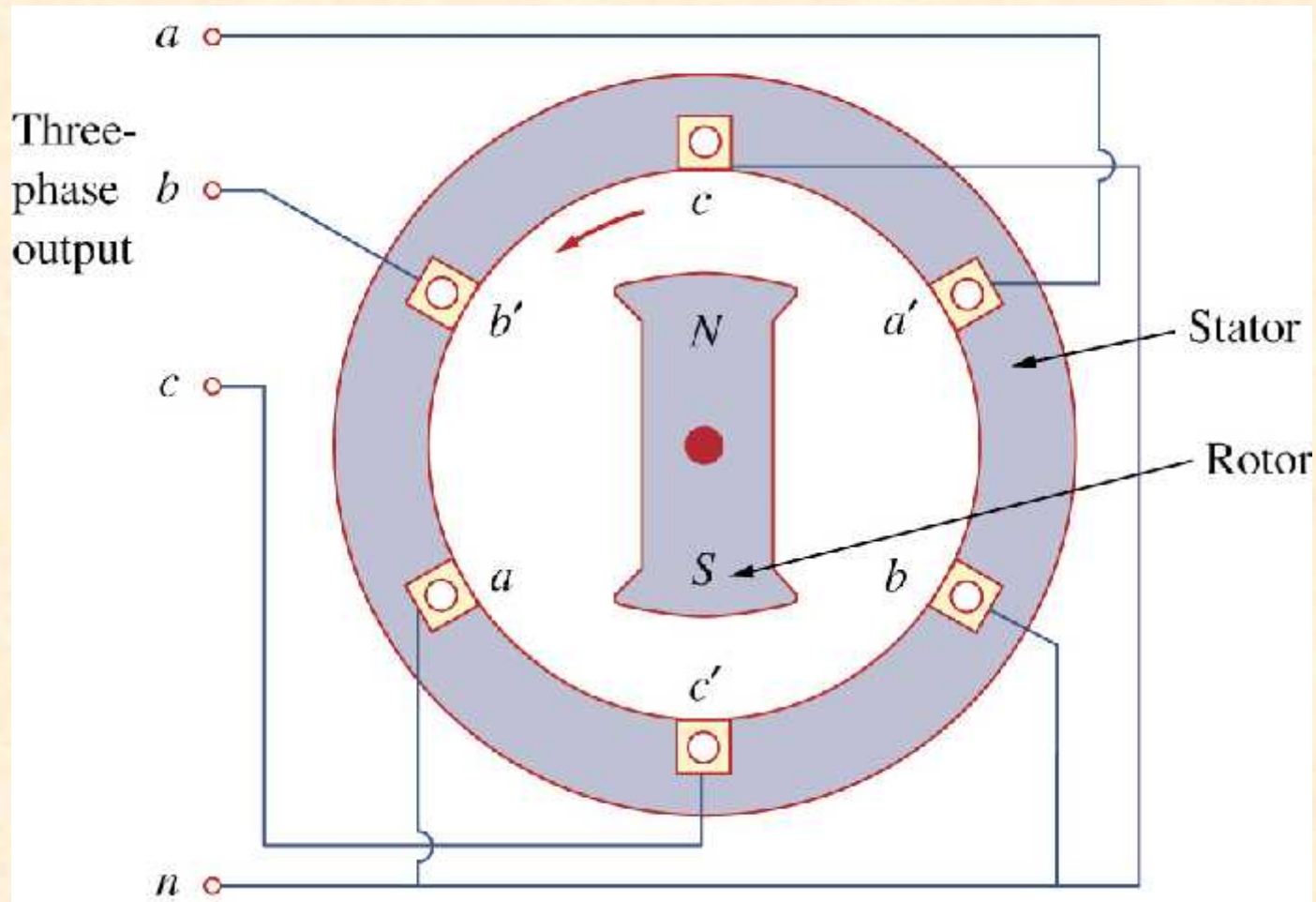


Three-Phase Voltages

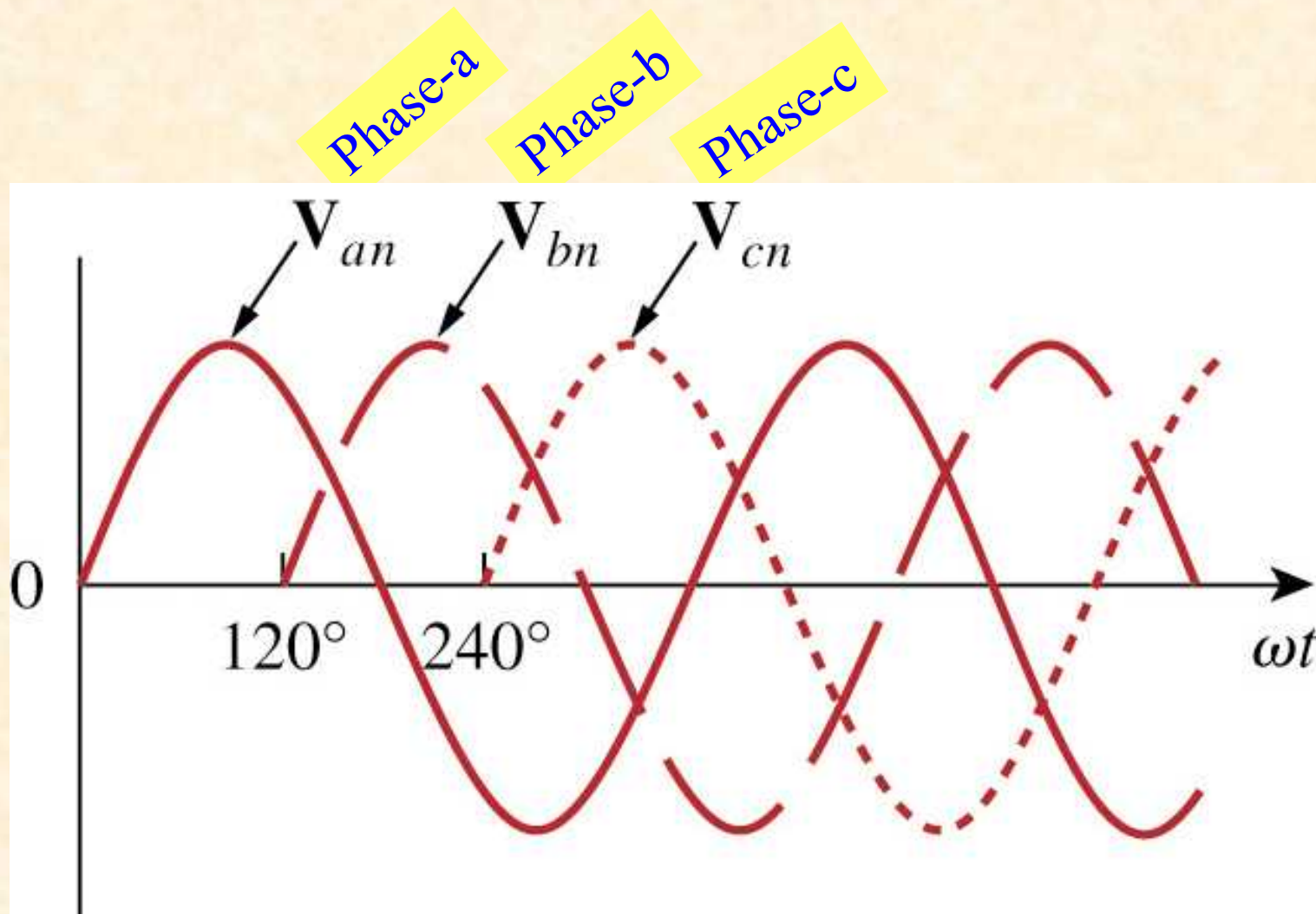


Basic Three-Phase Circuit

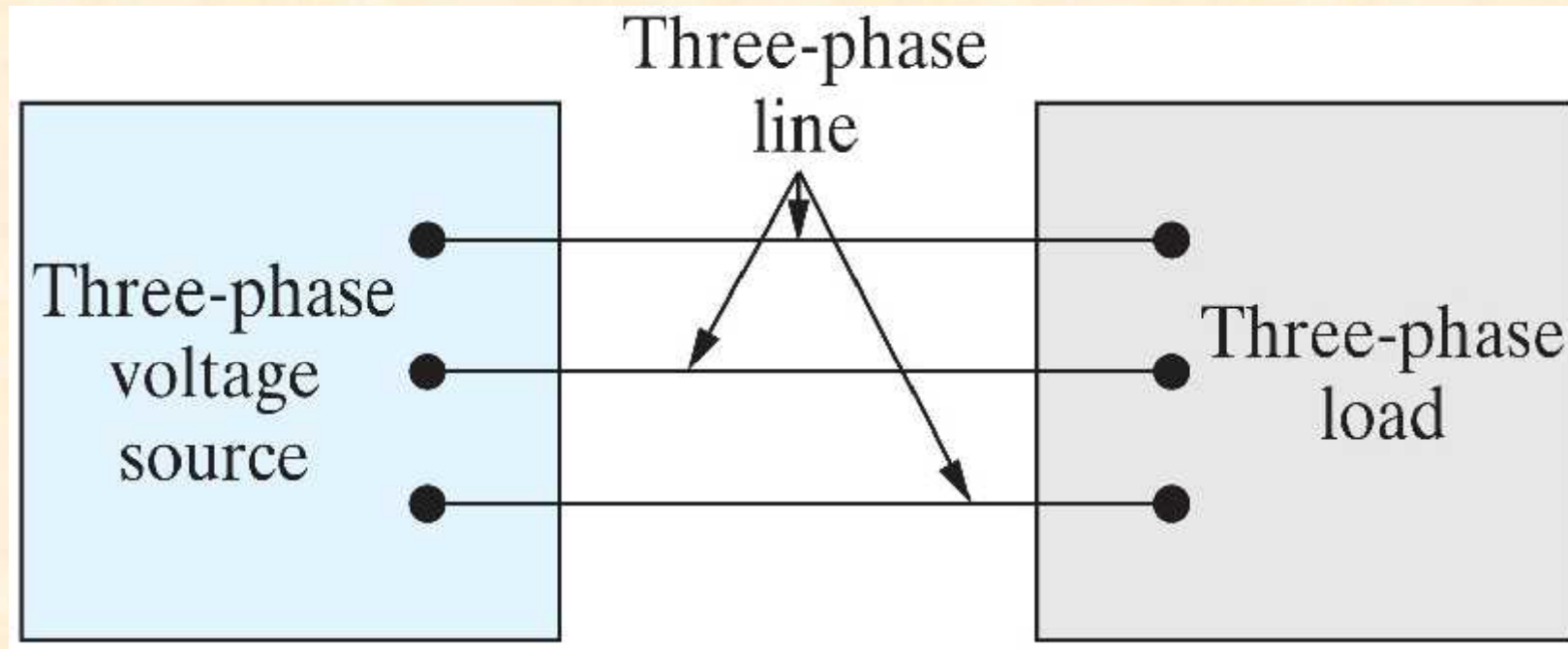

Three-Phase Voltages Sources

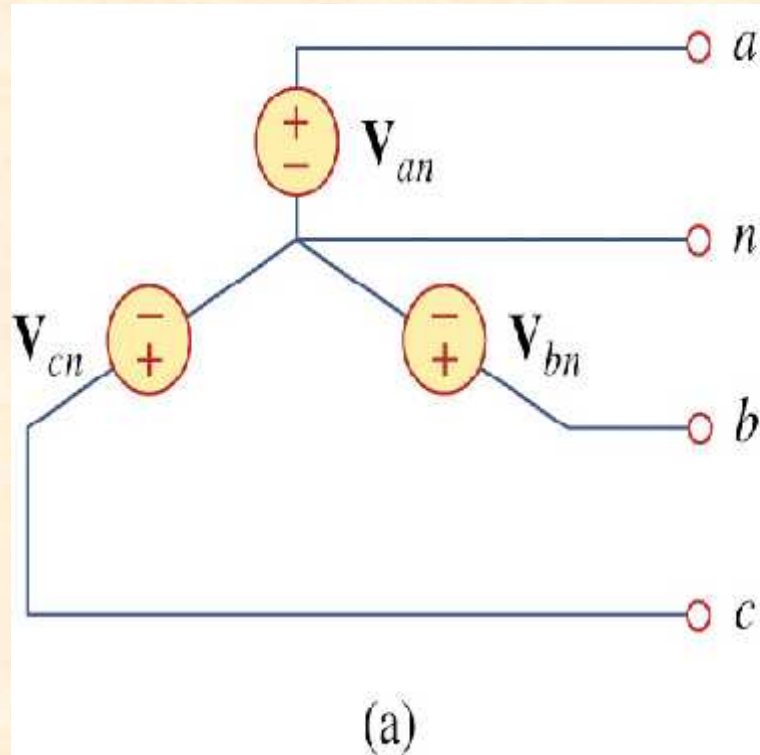

Y-connected Source

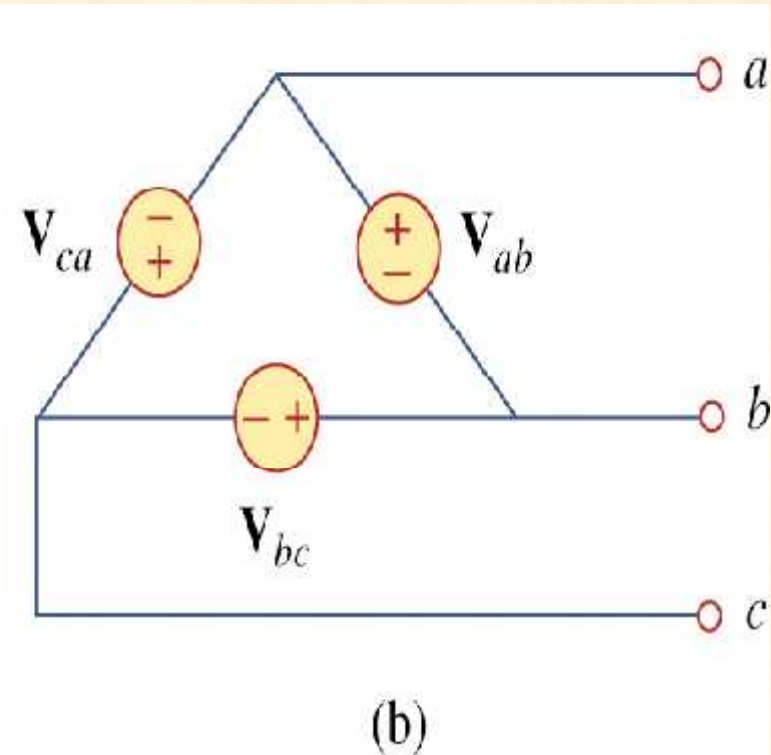


D-connected Source




Balanced Three-Phase Voltages Sources

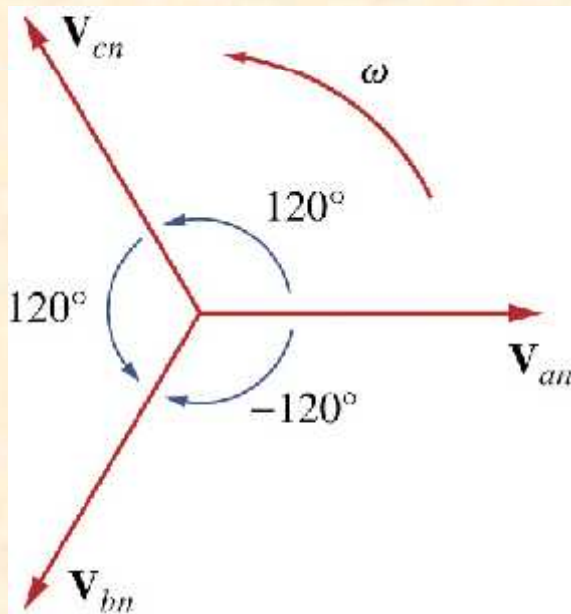- **Balanced phase voltages** are equal in magnitude and are out of phase with one another by **120** degrees
- Phase voltages sum up to zero ($V_{an} + V_{bn} + V_{cn} = 0$)
- There are **two possible combinations**:



abc or (+) sequence

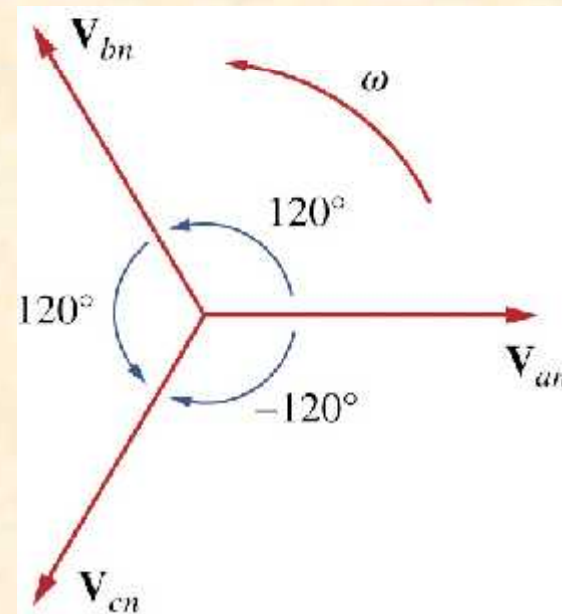

acb or (>) sequence



Balanced Three-Phase Voltages

$$v_{an}(t) = V_M \cos(\check{S} t)$$

$$v_{bn}(t) = V_M \cos(\check{S} t - 120^\circ)$$

$$v_{cn}(t) = V_M \cos(\check{S} t - 240^\circ) = V_M \cos(\check{S} t + 120^\circ)$$

$$V_{an} = V \angle 0^\circ$$

$$V_{bn} = V \angle -120^\circ$$

$$V_{cn} = V \angle +120^\circ$$

POSITIVE SEQUENCE

$$V_{an} = V \angle 0^\circ$$

$$V_{bn} = V \angle +120^\circ$$


$$V_{cn} = V \angle -120^\circ$$

NEGATIVE SEQUENCE




Balanced Three-Phase Load Configurations

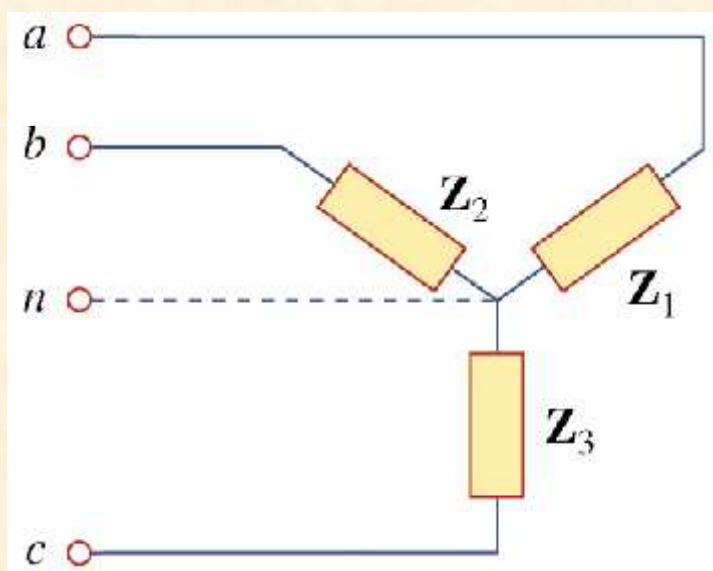➤ A **balanced three-phase load** is one in which the phase impedances are equal in magnitude and in **phase**



Y-connected Load

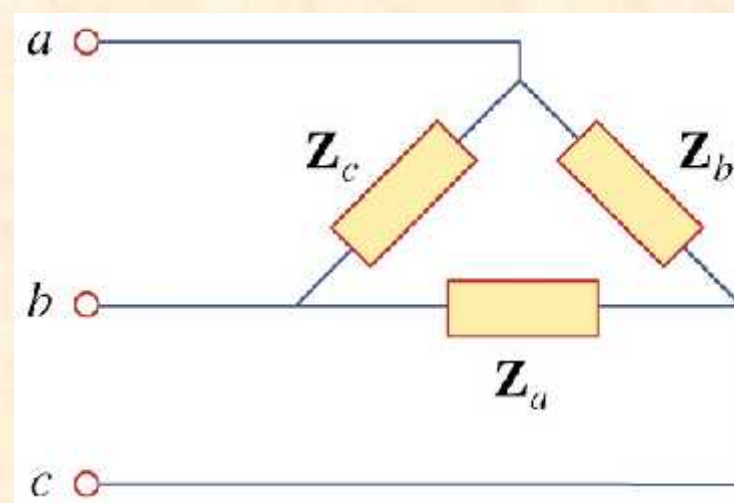

D-connected Load



Source-Load Connection

SOURCE	LOAD	CONNECTION
Wye	Wye	Y-Y
Wye	Delta	Y-U
Delta	Delta	U- U
Delta	Wye	U-Y



Three-Phase Quantities

QUANTITY	SYMBOL
Phase current	I_{ϕ}
Line current	I_L
Phase voltage	V_{ϕ}
Line voltage	V_L



Phase Voltages and Line Voltages & Currents

- ❑ Phase voltage, (V_ϕ) is measured between the neutral and any line: line to neutral voltage
- ❑ Line voltage, (V_L) is measured between any two of the three lines: line to line voltage
- ❑ Line current, (I_L) is the current in each line of the source or load
- ❑ Phase current, (I_ϕ) is the current in each phase of the source or load

